

Fall-2020
Final Exam

Name: Md. Selayman Hossain

ID : 1931565642

Sec: 08

Course: CSE231 Lab

Date: 09.01.2021

Md. Solayman Hossain

1931565642

Ans. no. 1

$$\Rightarrow F(A, B, C) = \Sigma(0, 2, 6, 7)$$

A	B	C	F	Data Inputs
0	0	0	1	$I_0 = 1$
0	0	1	0	
0	1	0	1	$I_1 = 0$
0	1	1	0	
1	0	0	0	$I_2 = B$
1	0	1	0	
1	1	0	1	$I_3 = B$
1	1	1	1	

AC select bit	I_0	I_1	I_2	I_3
B'	1	0	0	0
B	1	0	1	1
Input Values	1	0	B	B

2 Truth Table

Clock	J	K	Q_{n+1}
0	x	x	Q_n
1	0	0	Q_n
1	0	1	0
1	1	0	1
1	1	1	$\overline{Q_n}$

(toggle)

Ch Table:

Q_n	J	K	Q_{n+1}
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	0

Excitation Table:

Q_n	Q_{n+1}	J	K
0	0	0	x
0	1	1	x
1	0	x	1
1	1	x	0

When Q_n and Q_{n+1} are 0/1 or 1/0.

We can conclude,
When

Q_n is 00; Q_{n+1} is also 00. That's why

it is only dependent of J and we place
don't care in K in the excitation table

Ans. no. 3

$$(1010)_2$$

$$1's \text{ complement } (0101)_2$$

$$\begin{array}{r} _2 \\ + _2 \\ \hline 2's \text{ complement} = (0110)_2 \end{array}$$

Now,

$$\begin{array}{r} (1100)_2 \\ + (0110)_2 \\ \hline 1010 \end{array}$$

$$\therefore (1100)_2 - (1010)_2 = (10)_2$$

A 4 bit adder-subtractor is a circuit that is capable of adding or subtracting 4 bit inputs. A way to mark inputs output as positive^{or} negative without using multiplexer on each bit is to use XOR gates to proceed each bit. In the circuit, we will use 4 XOR gates and 4-bit adder-subtractor. Here, we will input $m=1$ for subtract. In the adder, we will input A & $(B \oplus M)$ to get subtraction of B from A.


Ans. no. 4

We can add two 8 bit numbers using two IC 7483 4 bit adder IC. IC 7483 is a 4 bit parallel adder which consists of four interconnected full adder along with the look ahead. Here, IC adds the two four bit words along with input carry to produce a 4-bit sum and a one bit carry out. In first adder, the carry input is supposed to be 0. Hence the carry in pin of IC is connected to the ground. This carry out of adder-1 is connected to Cin input of Adder-2. The second adder adds this carry and the four bits of numbers to produce sum along with final carry out bit Cout. Thus, we can use two IC 7438 to add two 8 bit numbers.

Md. Soleyman Hossain

1931565642

Ans. No. 5

 

Excitation Table			
$Q(t)$	$Q(t+1)$	y	h
0	0	0	X
0	1	1	X
1	0	X	1
1	1	X	0

Present state		Input	Next state		output	Flip Flop Functions			
A	B	X	A	B	$y(t)$	γ_A	K_A	γ_B	K_B
0	0	0	1	1	0	1	X	1	X
0	0	1	0	1	0	0	X	1	X
0	1	0	1	1	0	1	X	X	0
0	1	1	0	0	0	0	X	X	1
1	0	0	1	0	0	X	0	0	X
1	0	1	1	1	1	X	0	1	X
1	1	0	1	0	0	X	0	X	1
1	1	1	1	0	1	X	0	X	1

Md. Solayman Hossain

1931565642

State equation

1	0	0	1	0	3	1	0
1	3	1	3	1	7	1	6

$$A (k+1) = \bar{X} + A$$

1	0	1	1	0	3	1	2
0	3	1	5	0	7	0	6

$$B (k+1) = \bar{A} \bar{X} + \bar{B} X$$

K-map

$\Sigma_A K_A$

1	0	0	1	0	3	1	2
X_4	X_5	X_7	X_6				

$$\therefore \Sigma_A = \bar{X}$$

x_0	x_1	x_3	x_2
04	15	07	06

$$\therefore K_A = 0$$

$\Sigma_B K_B$

1	0	1	1	X_3	X_2
0	4	1	5	X_7	X_6

$$\therefore \Sigma_B = \bar{A} + X$$

X_0	X_1	1	3	0	2
X_4	X_5	1	7	1	1

$$\therefore K_B = X + A$$

Ans. no. 2

Y_k flip-flop is the same as that of the Y_k when Y and K are replaced by Q and Q (Next) respectively, except for the indeterminate case.

Here, in the Y_k excitation table, there is a don't care term in K column. That means whether the input is 1 or 0. According to characteristic table, Q refers to the next state and Q (next) refers to Q after the occurrence of the clock pulse.

Here, the flip-flop shows that the next state is equal to the present state 0.

That's why K 's value is don't care meaning 0 or 1.

Q	Q (Next)	Y	K
0	0	0	X

