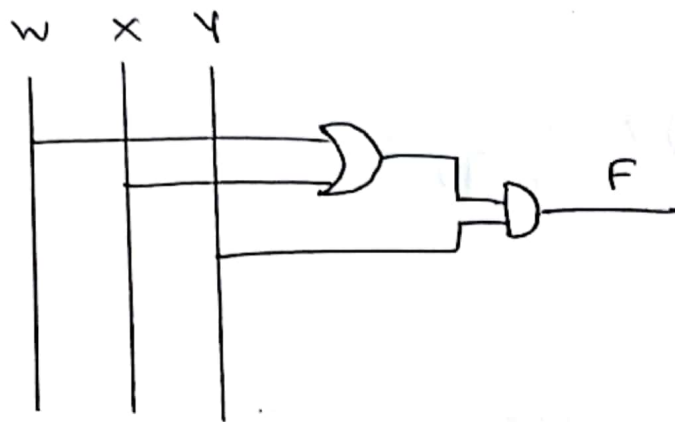


Name: Md. Rifat Ahmed

ID: 1931725042

Section: 8

9) $F(w, x, y) = (w + x) y$



Drawing the circuit using NAND gates only;

